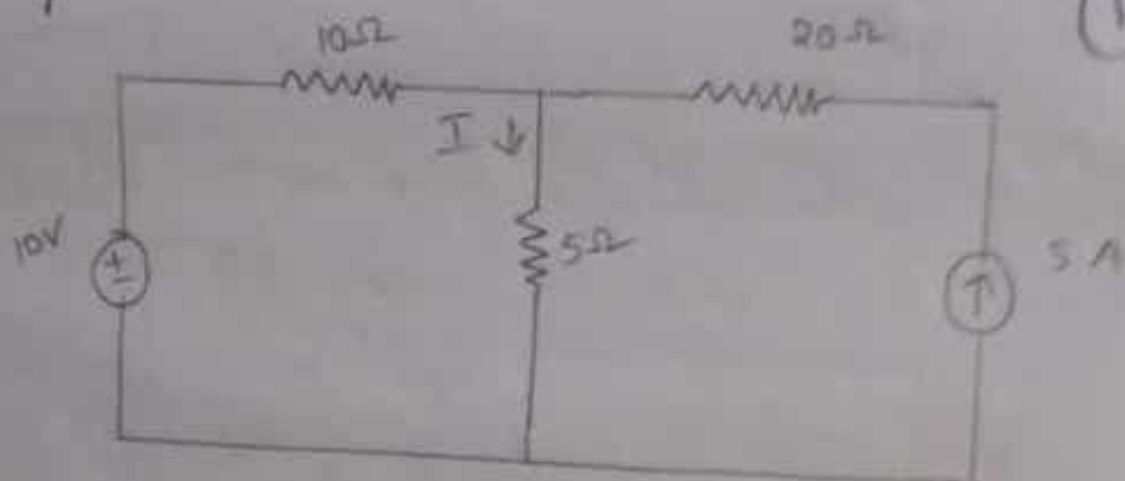


→ Super position theorem:- In a linear networks, with several independent sources. The response in a particular branch when all the sources acting simultaneously is equal to the algebraic sum of individual responses by taking one source at a time.

* Find the current in 5Ω by using super position theorem.




Procedure:-

- Select a single source alone then replace all the voltage sources by a short circuit and all the current sources by a open circuit; Do not disturb dependent sources.
- find voltage or current in a required branch
- Repeat the above steps for each independent source

Case (i): Take 10V as alone and 5A current source is open circuited.

9

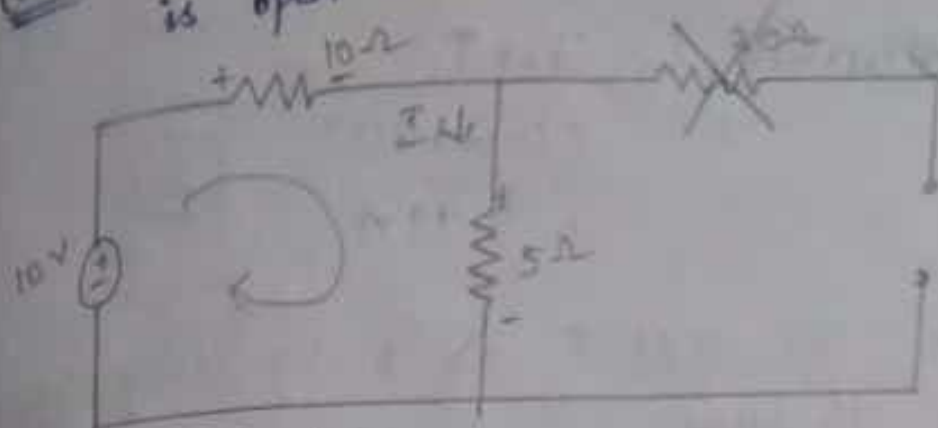

According to KVL,

$$+10 - 10I_1 - 5I_1 = 0$$

$$\Rightarrow 10 - 15I_1 = 0$$

$$10 = 15I_1$$


$$I_1 = \frac{10}{15}$$

$$I_1 = 2/3$$

$$\boxed{I_1 = 0.66A}$$

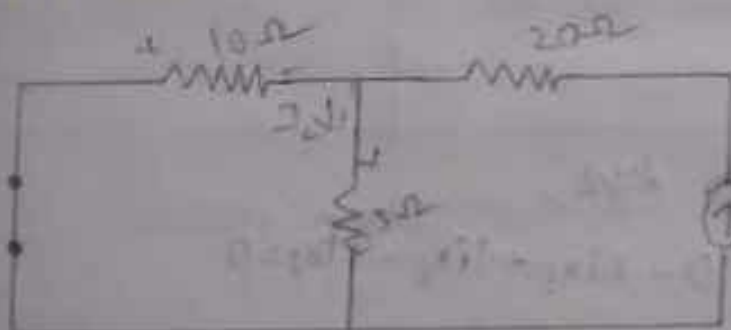(2)

Case (ii): Take 5A as alone and 10V voltage source is short circuited.



From the current division rule,

$$I_2 = I \left(\frac{R_1}{R_1 + R_2} \right) \text{ Here } I = 5A, R_1 = 10\Omega \text{ \& } R_2 = 5\Omega$$

$$I_2 = 5 \left(\frac{10}{10+5} \right)$$

$$I_2 = 5 \times \frac{10}{15} \Rightarrow I_2 = \frac{10}{3} = 3.3A$$


$$I_2 = 3.3 \text{ A}$$

10


$$\begin{aligned} \therefore \text{Total current } I &= I_1 + I_2 \\ &= 0.66 + 3.33 \\ &= 3.99 \text{ A} \end{aligned}$$

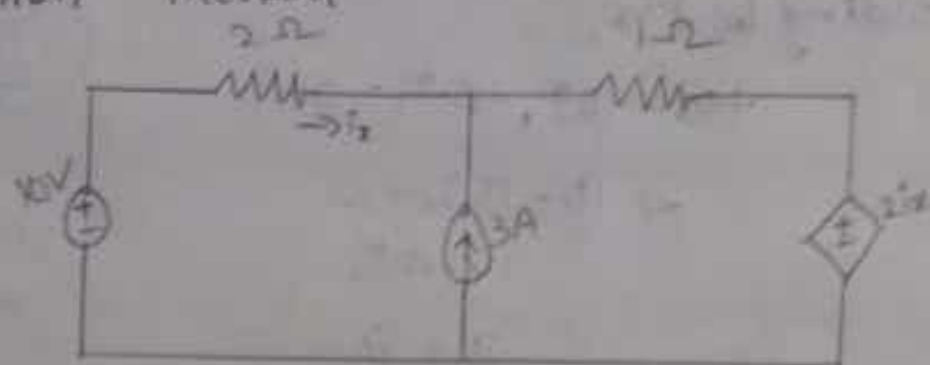(3)

* Determine the current i_x by using superposition theorem



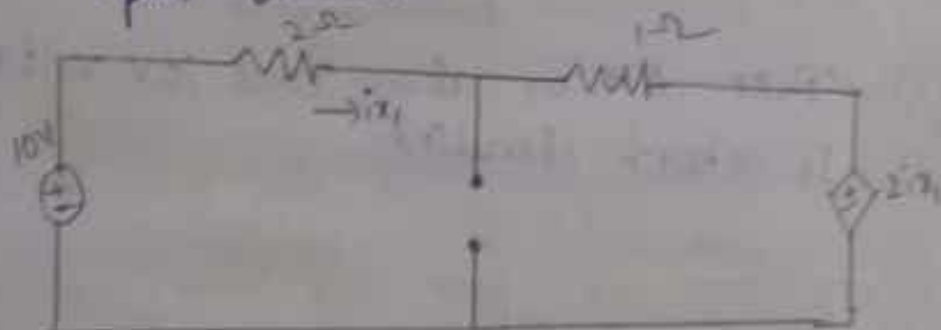Case (i):- Taking 10V source as alone and 3A is open-circuited



According to KVL,

$$+10 - 2i_{x1} - 1i_{x1} - 2i_{x1} = 0$$


$$10 - 5i_{x1} = 0$$

$$10 = 5i_{x1}$$

$$i_{x1} = \frac{10}{5}$$

$$i_{x1} = 2 \text{ A}$$

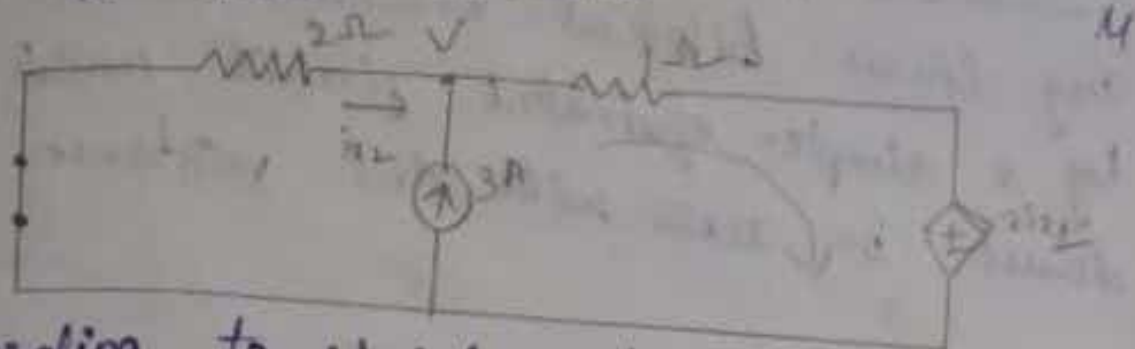Case (ii): Take. $3A$ is an alone, $10V$ voltage source is short circuited.



According to Nodal analysis.

$$i_{x2} + 3 = \frac{V - 2i_{x2}}{1} \quad (1)$$

$$\Rightarrow i_{x2} + 3 = V - 2i_{x2}$$

$$\Rightarrow V = 3i_{x2} + 3$$

$$V = 3(i_{x2} + 1) \rightarrow (1)$$

Here, Applying KVL,

$$2i_{x2} + V = 0$$

$$\Rightarrow \boxed{V = -2i_{x2}} \rightarrow (2)$$

Substitute eqn (2) in eqn (1)

$$-2i_{x2} = 3(i_{x2} + 1)$$

$$-2i_{x2} = 3i_{x2} + 3 \Rightarrow -5i_{x2} = 3$$


$$\boxed{i_{x2} = -\frac{3}{5}} \Rightarrow i_{x2} = -0.6A$$

$$\text{Total current} = i_{x1} + i_{x2}$$

$$= 2 - 0.6$$

$$= 1.4A$$

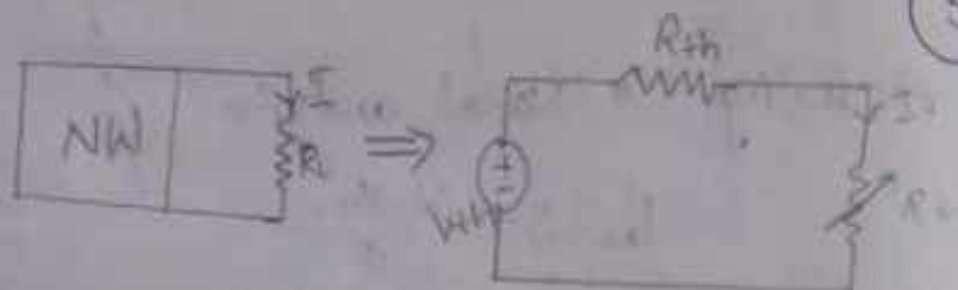
→ Thevenin's theorem: - Thevenin's theorem states that any linear bilateral network can be replaced by a simple equivalent circuit consists of voltage source in series with the resistance.




Procedure:

- Remove the resistance through which desired current flows.
- Find the open circuit voltage between two terminals that is called Thevenin's Voltage.
- Find the thevenin's equivalent resistance by considering the all voltage sources are short circuited and current sources are open circuited.
- Draw the equivalent thevenin's circuit.

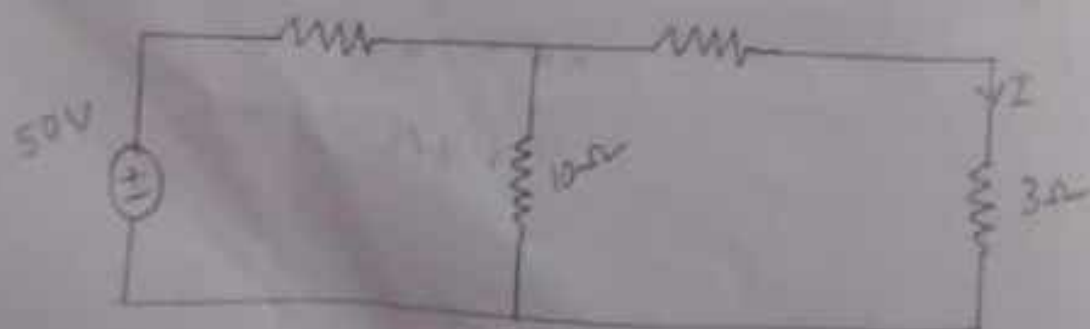* Find the current in 3Ω resistor using thevenin's theorem



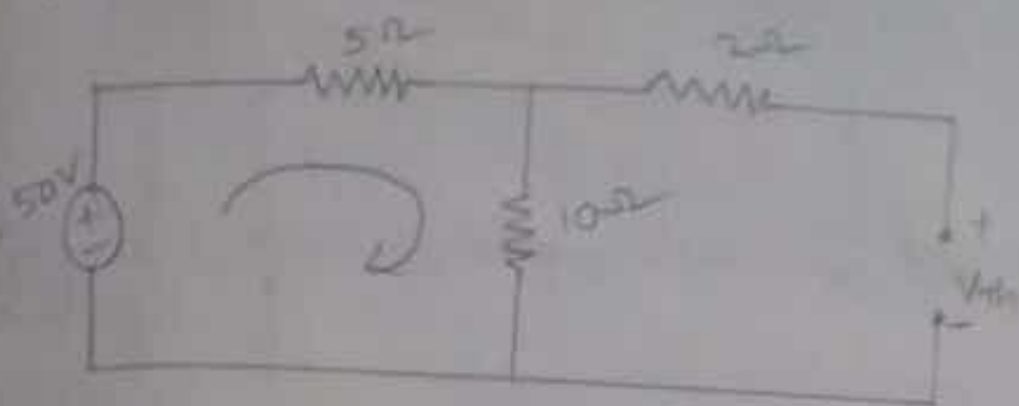After removing the desired current flows in the resistor $1\Omega, 3\Omega$



13

By Applying KVL, we get

(6)

$$50 - 5I_1 - 10I_1 = 0$$


$$\Rightarrow 50 - 15I_1 = 0$$

$$15I_1 = 50$$

$$I_1 = \frac{50}{15}$$

$$I_1 = 3.33 \text{ A}$$
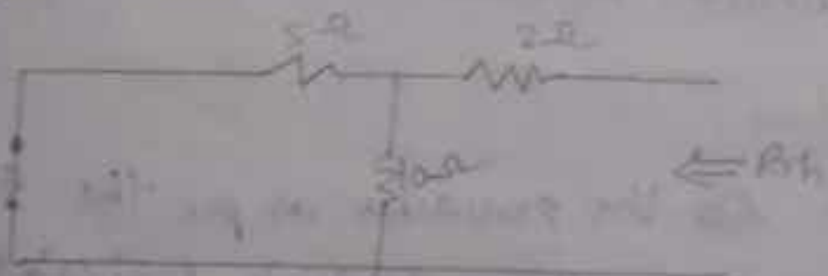
$$V_{th} = V_{10\Omega} = 3.33 \times 10 = 33.3 \text{ V}$$



$$R_{th} = \frac{1}{5} + \frac{1}{10}$$


$$= \frac{50}{15} + 2$$

$$= 3.33 + 2$$

$$R_{th} = 5.3 \Omega$$

Equivalent thevinin's circuit:-

14

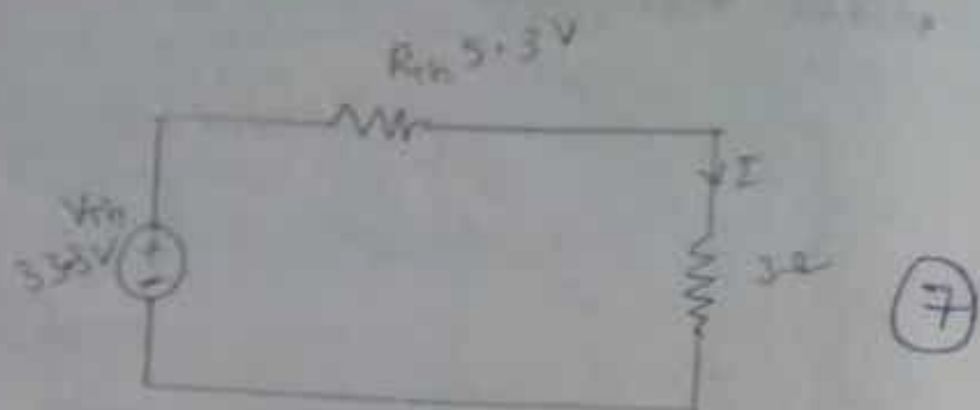


$$I = \frac{V}{R} = \frac{33.3}{5.3 + 3} = \frac{33.3}{8.3}$$

$$\boxed{I = 4.01 A}$$

→ Norton's theorem:- Any linear bi-lateral network can be replaced by a simple equivalent circuit consisting of a single current source in parallel with the resistance. Norton's is a converse of thevinin's theorem.


Procedure:-

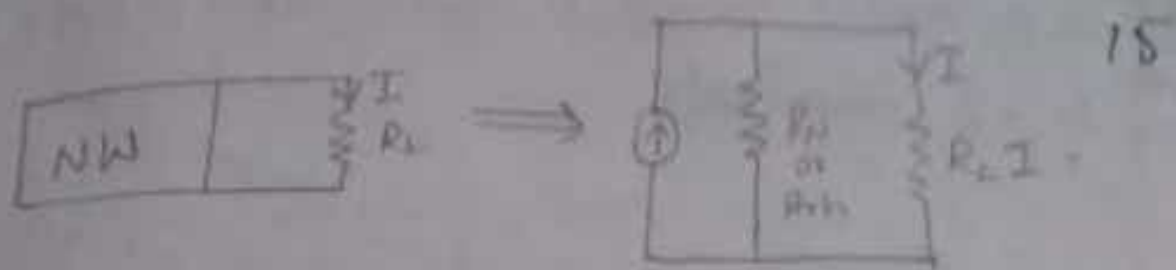- Do the procedure as per the thevinin's theorem
- Draw the thevinin's equivalent circuit.
- By using source transformation convert V_{th} to I_{sc} (or) I_N and R_{th} to R_N
- Now draw Norton's equivalent circuit.




for the above problem, Thevenin's equivalent circuit


is:

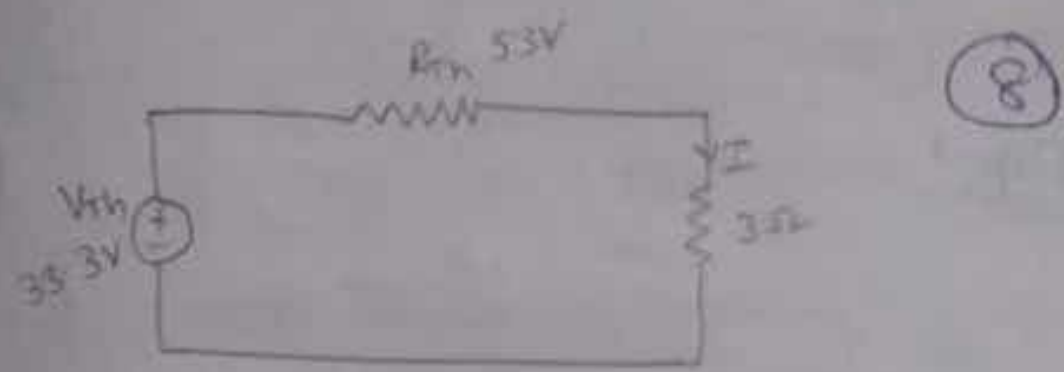

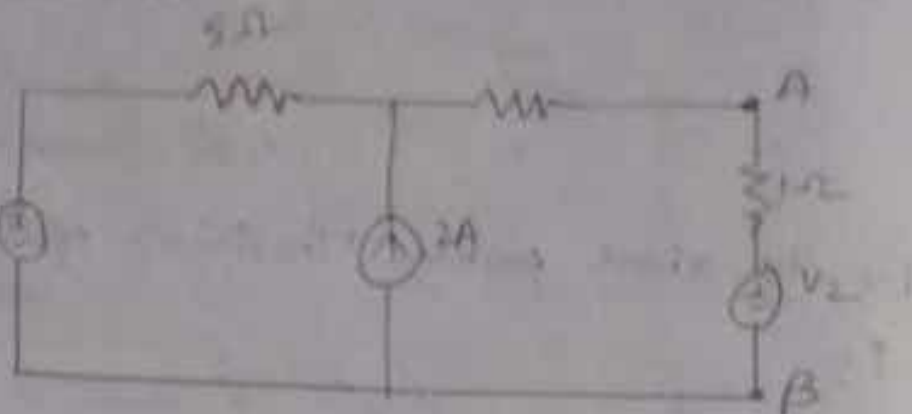
Q7) Find the thevenin's equivalent circuit between A & B terminals. 16



Step - 1

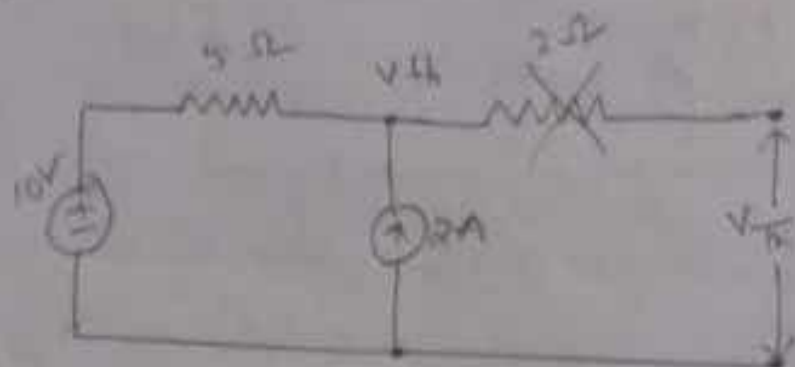

By using source transformation

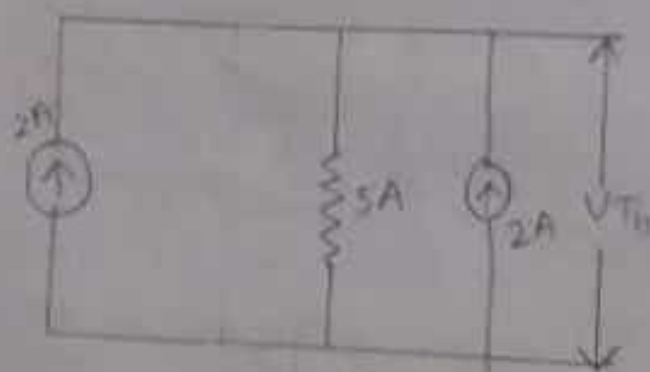


Here, in the above circuit 2A & 2A current sources are in parallel. So it will be 4A.



$$\therefore V_{Th} = 4 \times 5 = 20 \text{ V}$$


1A

Step 2

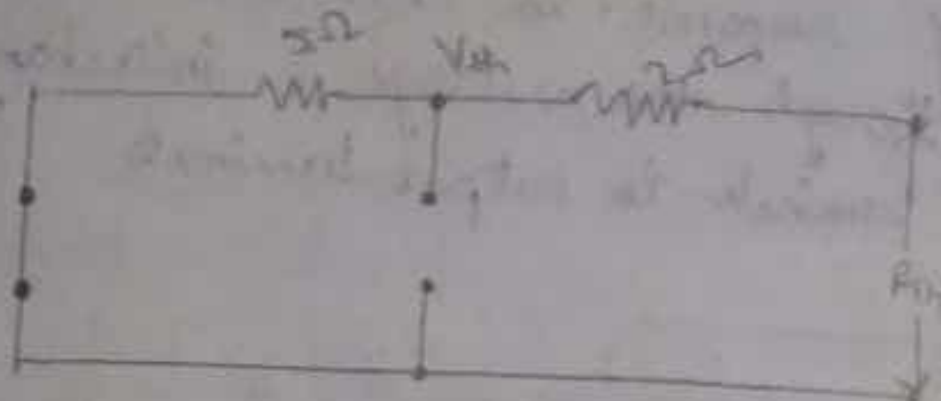

$$R_{Th} = 5\Omega + 2\Omega = 7\Omega$$

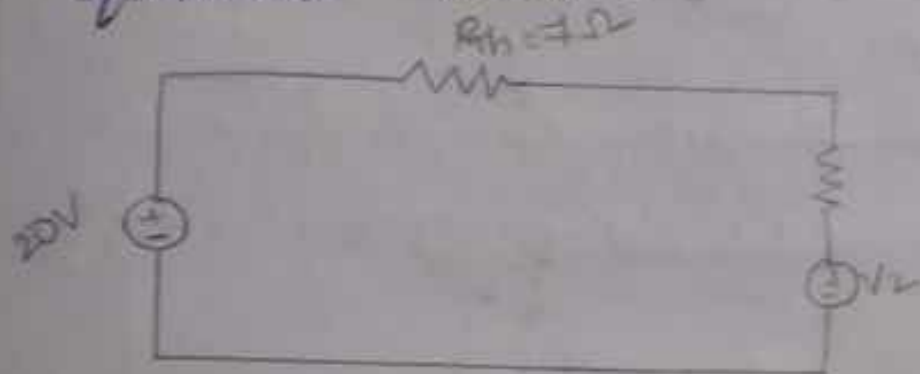\therefore Equivalent Thevenin's circuit is




Draw the norton's equivalent circuit for the above problem.




Reciprocity theorem

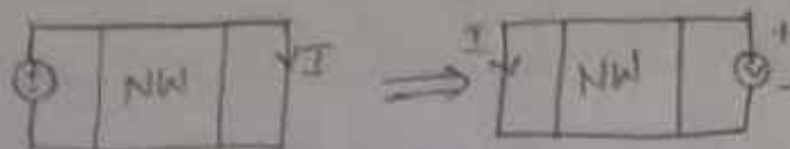In any linear bilateral network the ratio of response to excitation is constant even though the voltage is interchanged from input terminals to output terminals



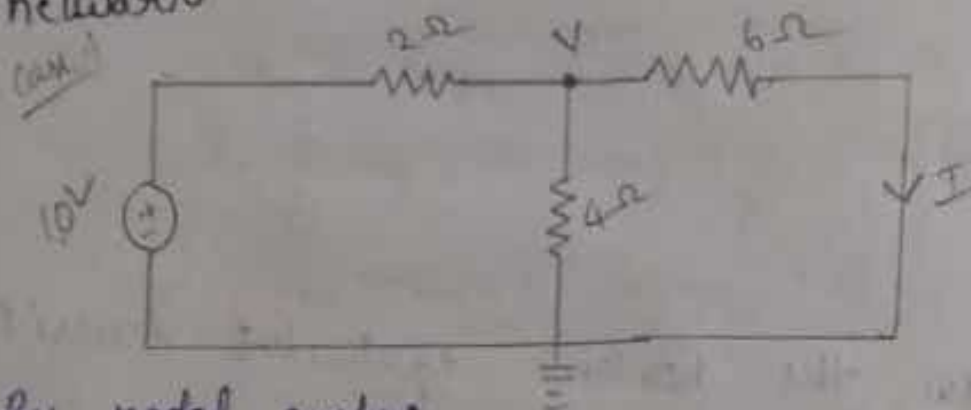* Verify reciprocity theorem for the following network.



Sol: By nodal analysis

$$\frac{V-10}{2} + \frac{V}{4} + \frac{V}{6} = 0$$

$$\frac{6V-60+3V+2V}{12} = 0$$


$$6V-60+5V = 0$$

$$11V = 60$$

$$V = \frac{60}{11}$$

$$\boxed{V = 5.45V}$$
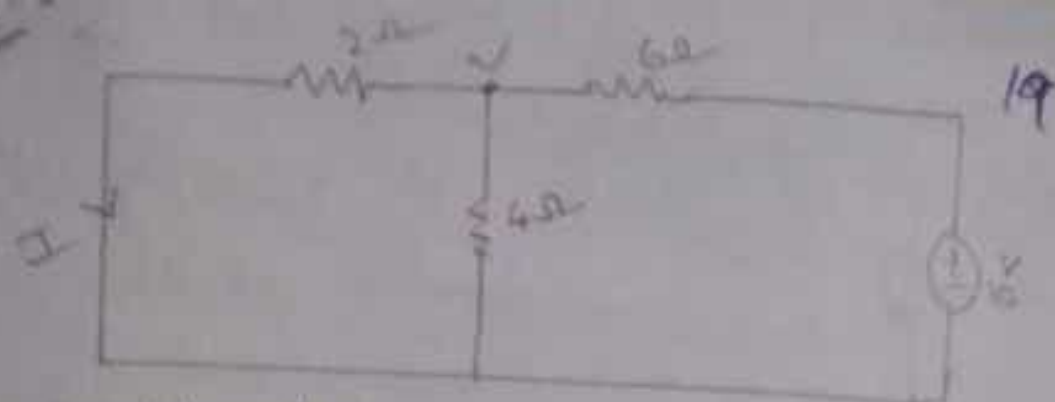
$$V = IR \Rightarrow I = \frac{V}{R} = \frac{5.45}{6} = 0.908A$$



By nodal analysis,

$$\frac{V}{2} + \frac{V}{4} + \frac{V-10}{6} = 0$$

$$\frac{6V + 3V + 2V - 20}{12} = 0$$

$$11V = 20 \Rightarrow V = \frac{20}{11} = 1.81V$$


$$I = \frac{V}{R} = \frac{1.81}{2} = 0.9A$$

Here the current flows in case (i), case (ii) are equal. So it satisfies the reciprocity theorem.

Maximum power transfer theorem:-

Maximum power transfer theorem states that maximum power transmitted from a source to load when ~~load~~ source resistance is equal to the load resistance.

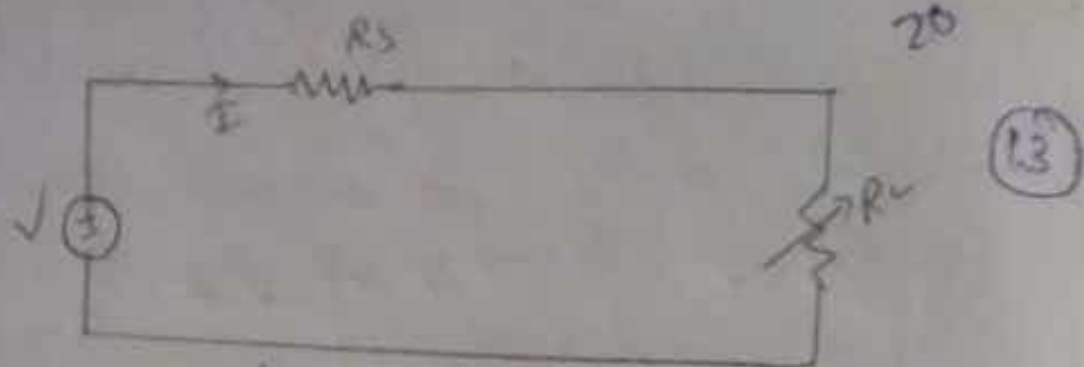"Prove that source resistance is equal to the load resistance."



From the above circuit, current $I = \frac{V}{R_S + R_L}$

Power delivered to the load $P = I^2 R_L$

$$P = \frac{V^2}{(R_S + R_L)^2} \cdot R_L$$

To get the maximum power for finding the value of R_L , Differentiate P with respect to R_L on both sides and equating with to zero.

$$P = \frac{V^2 R_L}{(R_S + R_L)^2}$$

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left(\frac{V^2 R_L}{(R_S + R_L)^2} \right) = 0$$

$$\Rightarrow \frac{(R_S + R_L)^2 \cdot V^2 - V^2 R_L (2(R_S + R_L))}{(R_S + R_L)^4} = 0$$


$$\Rightarrow (R_S + R_L)^2 \cdot V^2 - V^2 R_L (2(R_S + R_L)) = 0$$

$$\Rightarrow V^2 (R_S + R_L) \{ (R_S + R_L) - 2R_L \} = 0$$

$$\Rightarrow R_S + R_L - 2R_L = 0$$


$$\Rightarrow R_S - R_L = 0 \Rightarrow \boxed{R_S = R_L}$$

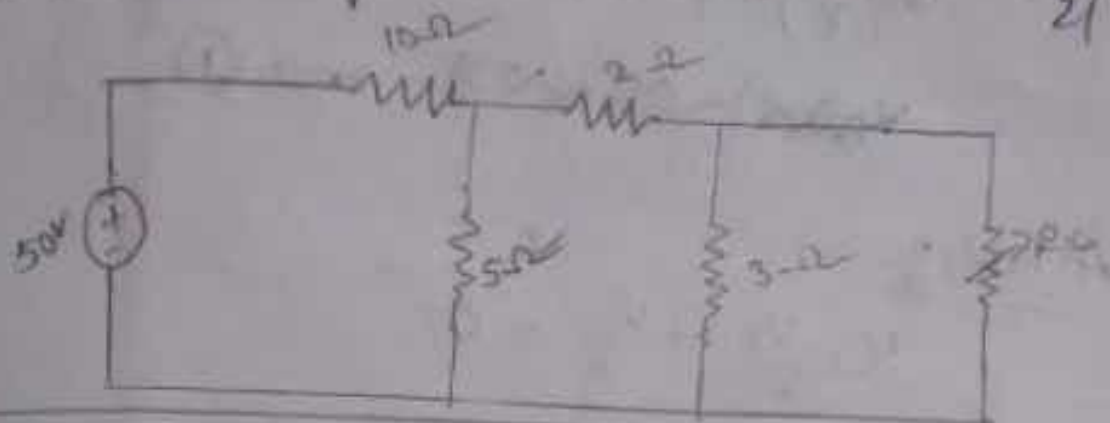* Determine the load resistance to receive maximum power from source and also find the minimum power delivered to the load.



Procedure:-

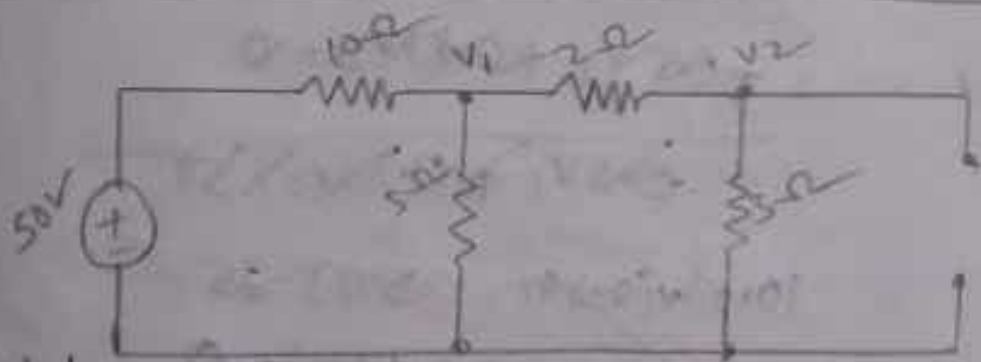- Open circuit R_L
- find out the thevinin's voltage at the open terminals.
- find out the R_{th}
- Draw the thevinin's equivalent circuit



At node 1

$$\frac{V_1 - 50}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1}{10} - \frac{50}{10} + \frac{V_1}{5} + \frac{V_1}{2} - \frac{V_2}{2} = 0$$

$$V_1 \left(\frac{1}{10} + \frac{1}{5} + \frac{1}{2} \right) - \frac{V_2}{2} = 5$$

$$V_1 \left(\frac{2+4+10}{20} \right) - \frac{V_2}{2} = 5$$

At node 2

$$\left(\frac{V_1 + 2V_1 + 5V_1}{10} \right) - \frac{V_2}{2} = 5$$

22

$$\frac{8V_1}{10} - \frac{V_2}{2} = 5$$

(15)

$$\frac{8V_1 - 5V_2}{10} = 5$$

$$8V_1 - 5V_2 = 50 \rightarrow (1)$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} = 0$$

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{3} = 0$$

$$\frac{V_2}{2} + \frac{V_2}{3} - \frac{V_1}{2} = 0$$

$$\frac{3V_2 + 2V_2 - 3V_1}{6} = 0$$

$$5V_2 - 3V_1 = 0$$

$$-3V_1 + 5V_2 = 0 \rightarrow (2)$$

Solve (1) & (2), (15).

$$-3V_1 + 5V_2 = 50$$

$$5V_1 - 5V_2 = 0$$

$$5V_1 = 50$$

$$\boxed{V_1 = 10}$$


put $V_1 = 10$ in eq (2)

$$-3(10) + 5V_2 = 0$$

$$\Rightarrow -30 = -5V_2$$

$$\boxed{V_2 = 6}$$

$$\therefore V_1 = 10, V_2 = 6$$

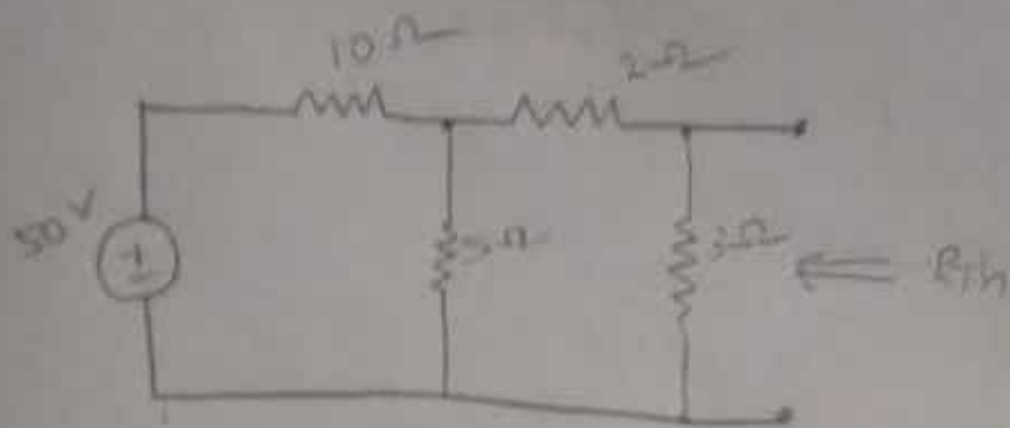

(16)

$$R_{eq} = \frac{50}{15} = 3.33$$

$$R_{eq} = 3.33 + 2 = 5.33$$

$$R_{eq} = \frac{5.33(3)}{3 + 5.33} = 1.91\Omega$$

$$\boxed{R_{th} = 1.91\Omega}$$

From maximum power transfer theorem

$$R_{th} = R_S = R_L = 1.91\Omega$$

Now

$$P = I^2 R_L$$

$$I = \frac{V}{R_S + R_L}$$


$$= \frac{6}{1.91 + 1.91}$$

$$= \frac{6}{3.82}$$

$$= 1.57\Omega$$

$$P = (1.57)^2 (1.9)$$

$$\boxed{P = 4.68 \text{ watts}}$$

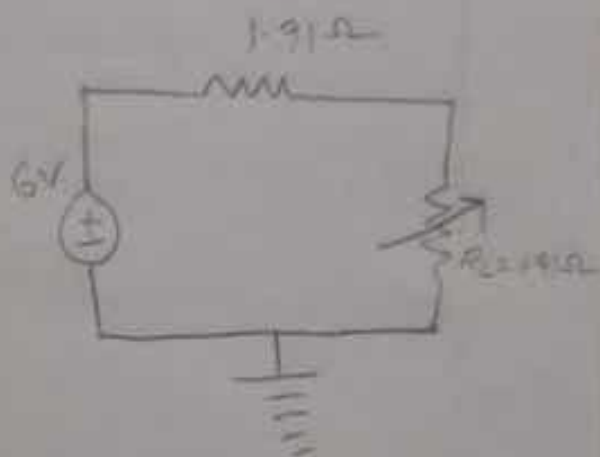

Power delivered to the load = 4.68W